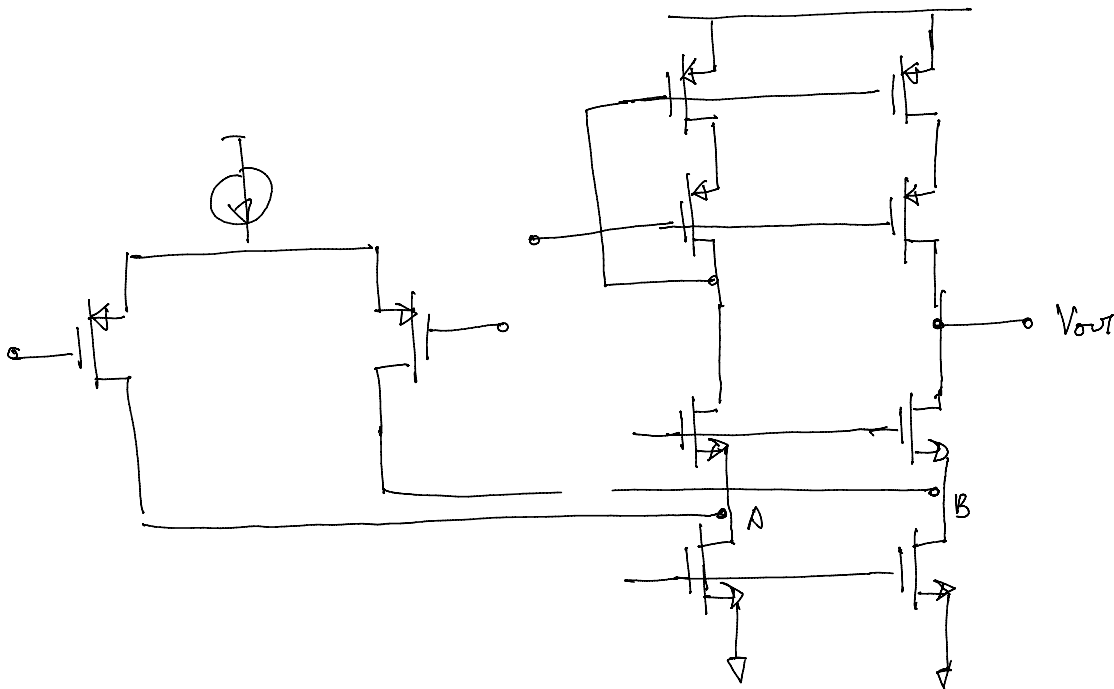



FOLDED CASCODE OPAMP ANALYSIS




→ Question is how much small signal current goes up on nodes A & B.

→ Are nodes A & B actually low impedance on looking up so that we have minimum current division on nodes A & B?

Let's simplify the circuit for analysis:


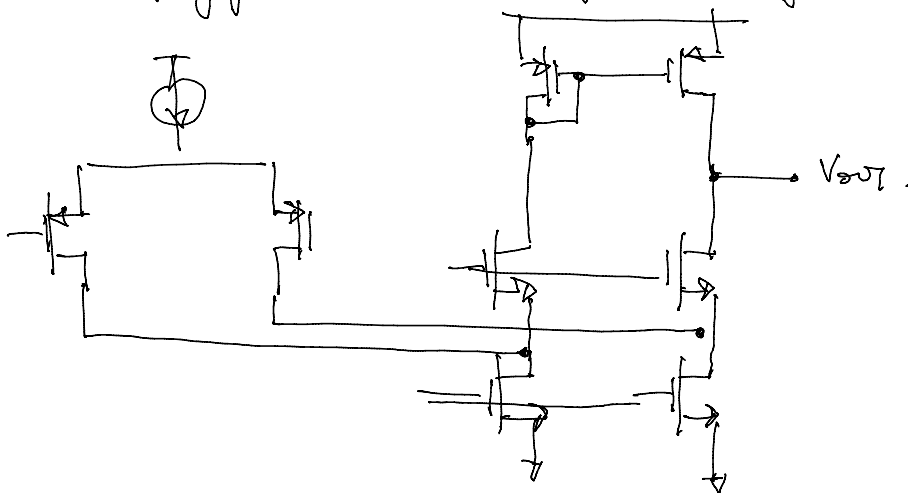


SMALL SIGNAL MODEL

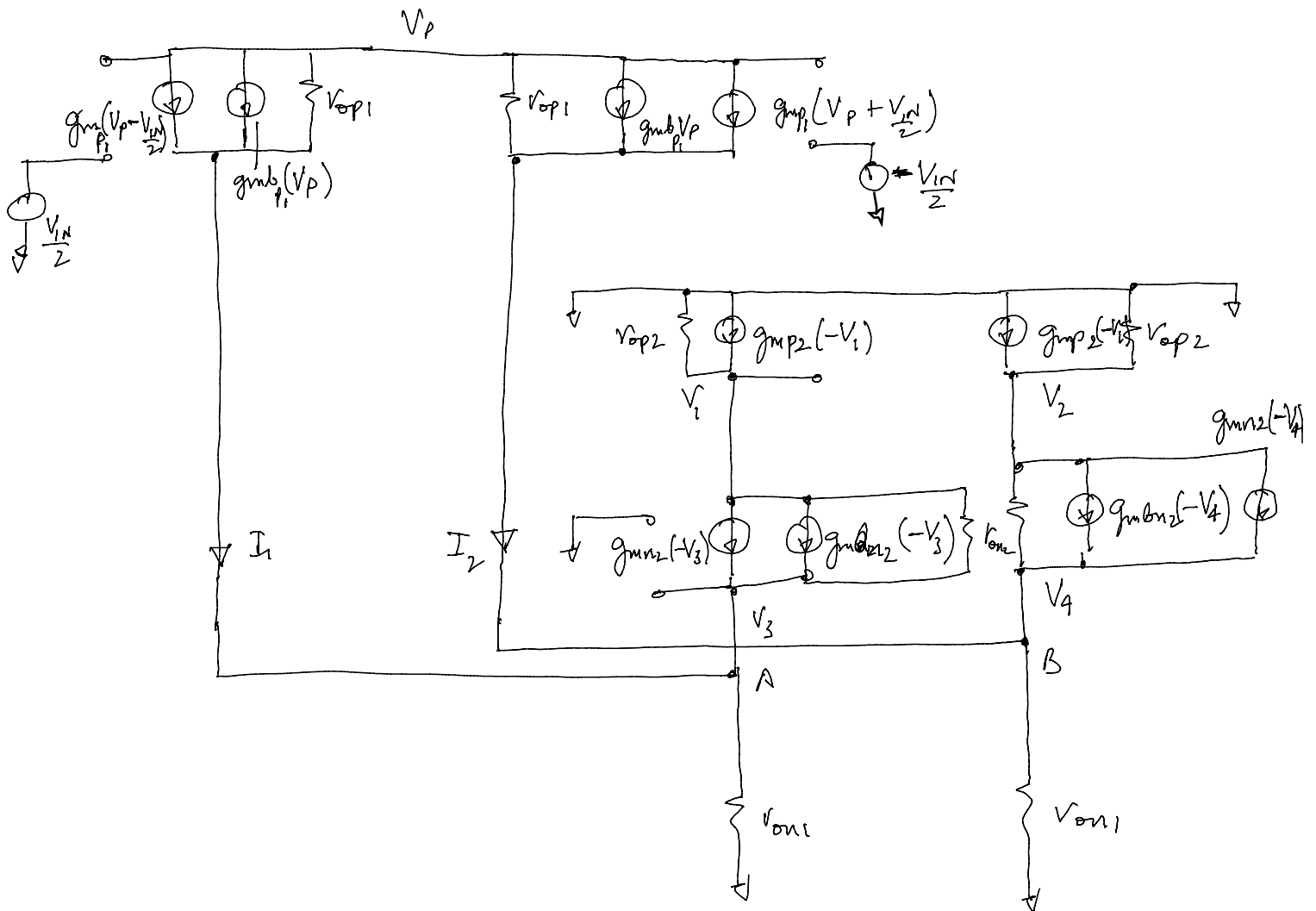

From this we see $I_1 = -I_2$

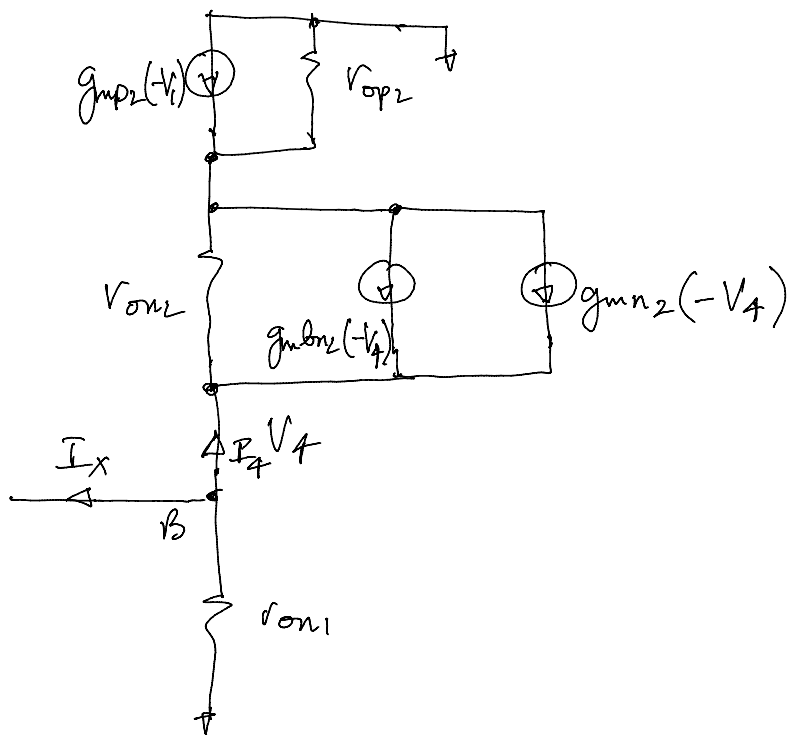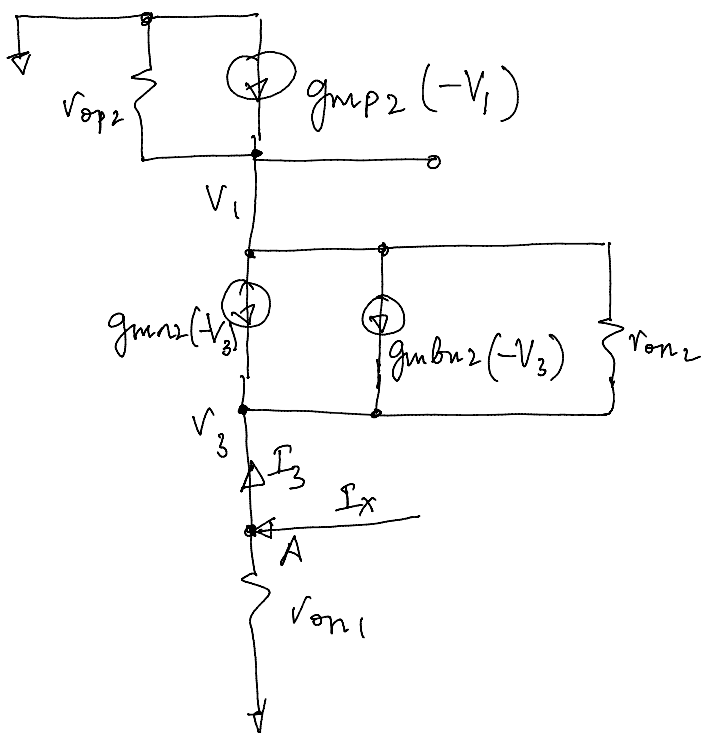Since we are interested in the impedances of nodes A and B let's simplify the circuit further based on this result to concentrate on A & B.



→ Combine g_{mn2} & g_{mbn2} → ~~G_{mn2}~~ G_{mn2}

$$I_3 = g_{mp2} V_1 + \frac{V_1}{r_{op2}} \Rightarrow V_1 = \frac{r_{op2}}{g_{mp2} r_{op2} + 1} I_3$$

Also $I_3 = \frac{r_{on1}}{r_{on1} + R_{in1}} I_x = K I_x$ $R_{in1} = \text{Resistance looking up at node A}$
 $= \frac{V_3}{I_3}$

$$R_{in1} = \frac{r_{on2} + \frac{r_{op2}}{g_{mp2} r_{op2} + 1}}{1 + r_{on2} G_{mn2}} = \frac{r_{on2} + r_{op2} || (1/g_{mp2})}{1 + r_{on2} G_{mn2}}$$

∴ $V_1 = B I_x$ where $B = \frac{r_{on1}}{r_{on1} + R_{in1}} \cdot \frac{r_{op2}}{g_{mp2} r_{op2} + 1}$

$$I_4 = g_{m2} B I_x + \frac{V_2}{r_{op2}} = A I_x + \frac{V_2}{r_{op2}}$$

$$\text{where } A = \frac{g_{m2} r_{op2}}{g_{m2} r_{op2} + 1} \frac{r_{on1}}{r_{on1} + R_{e1}}$$

$$R_{e1} = \frac{r_{on2} + \frac{r_{op2}}{g_{m2} r_{op2} + 1}}{1 + r_{on2} g_{m2}}$$

$$\therefore V_2 = (I_4 - A I_x) r_{op2}$$

$$\& I_4 = G_{m2} V_4 + \frac{V_4 - (I_4 - I_x A) r_{op2}}{r_{on2}}$$

$$R_{e2} = \frac{r_{on2} + r_{op2} (A + 1)}{G_{m2} r_{on2} + 1 - A \frac{r_{op2}}{r_{on1}}}$$

$$\text{where } A = \frac{g_{m2} r_{op2}}{g_{m2} r_{op2} + 1} \frac{r_{on1}}{r_{on1} + R_{e1}}$$

$$R_{e1} = \frac{r_{on2} + \frac{r_{op2}}{g_{m2} r_{op2} + 1}}{1 + r_{on2} G_{m2}}$$

If $g_{mp2} v_{op2} \gg 1$ & $k_{u1} \ll r_{on1} \rightarrow$ for nice amp to let all small signal current go up.

$$A \approx 1$$

$$R_{u2} = \frac{r_{on2} + 2r_{opL}}{g_{mnp2} r_{on2} + 1 - \frac{2r_{opL}}{2r_{on1}}}$$

$$A \rightarrow 1$$

\Rightarrow Thus the impedance on node B is more than on node A due to the control by I_x on node A

\Rightarrow on node A the impedance looking up (R_{u1}) was simply the impedance looking into the source of the transistor since this part is not affected by the other string in any way.

\Rightarrow For most of the current to go up on node A R_{u1} should be less

\Rightarrow For most of the current to go up on node B R_{u2} ~~should~~ should be less.