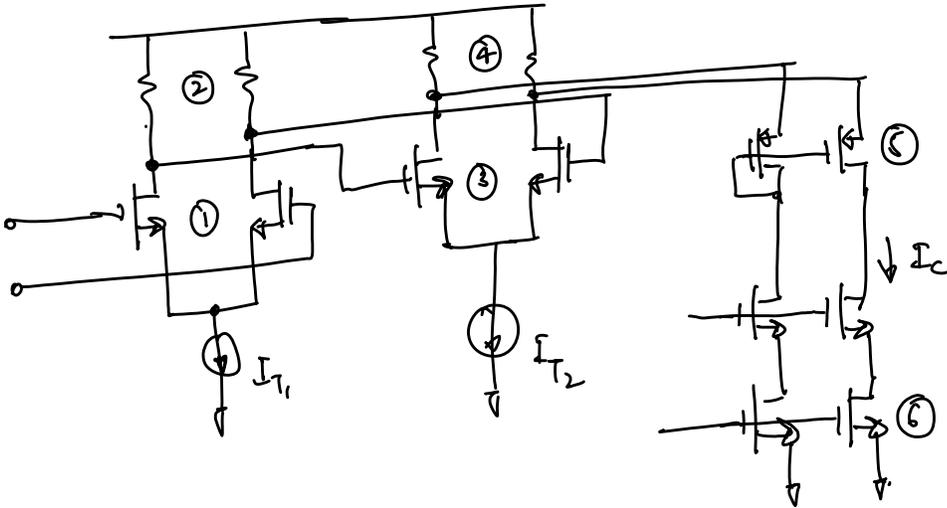


HS COMP OFFSET ANALYSIS



$$V_{OS1} = \Delta V_{TH1}$$

$$V_{OS2} =$$



$$\Delta V_{OUT} = \left(\frac{I_{T1}}{2} \left(R_2 - \frac{\Delta R_2}{2} \right) - \frac{I_{T1}}{2} \left(R_2 + \frac{\Delta R_2}{2} \right) \right)$$

$$= \frac{I_{T1}}{2} \Delta R_2 = g_{m1} R_2 V_{OS2}$$

$$\therefore V_{OS2} = \frac{I_{T1} \Delta R_2}{2 g_{m1} R_2}$$

$$V_{OS3} = \frac{\Delta V_{TH3}}{g_{m1} R_2}$$


$$g_{m1} R_2 g_{m3} R_4 V_{OS4} = \left(\left(I_C + \frac{I_{T2}}{2} \right) \left(R_4 - \frac{\Delta R_4}{2} \right) - \left(I_C + \frac{I_{T2}}{2} \right) \left(R_4 + \frac{\Delta R_4}{2} \right) \right)$$

$$= \left(I_C + \frac{I_{T2}}{2} \right) \Delta R_4$$

$$\text{or } V_{OS4} = \left(I_C + \frac{I_{T2}}{2} \right) \frac{\Delta R_4}{g_{m1} R_2 g_{m3} R_4}$$

$$V_{OS5} = \frac{\Delta V_{TH5}}{g_{m3} R_4 + g_{m1} R_2}$$

V_{OS6} :

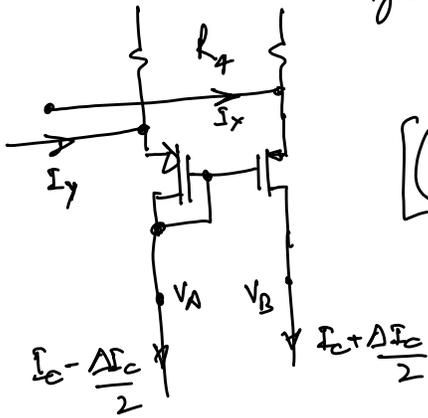

Ignoring Body Effect due to mismatched currents

$$V_A = V_B \therefore$$

$$\begin{aligned} \left[\left(I_c - \frac{\Delta I_c}{2} \right) - I_y \right] R_4 + V_{GS5} - \frac{\Delta V_{GS5}}{2} \\ = \left[\left(I_c + \frac{\Delta I_c}{2} \right) - I_x \right] R_4 + V_{GS5} + \frac{\Delta V_{GS5}}{2} \end{aligned}$$

$$(I_x - I_y) R_4 = \Delta I_c R_4 + \Delta V_{GS5}$$

$$\Delta V_{GS5} = \frac{\Delta I_c}{g_{m5}}$$

$$\therefore I_x - I_y = \Delta I_c + \frac{\Delta I_c}{g_{m5} R_4}$$

$$V_{OS6} = \Delta I_c \left(1 + \frac{1}{g_{m5} R_4} \right) \cdot \frac{1}{g_{m3}} \cdot \frac{1}{g_{m1} R_2}$$