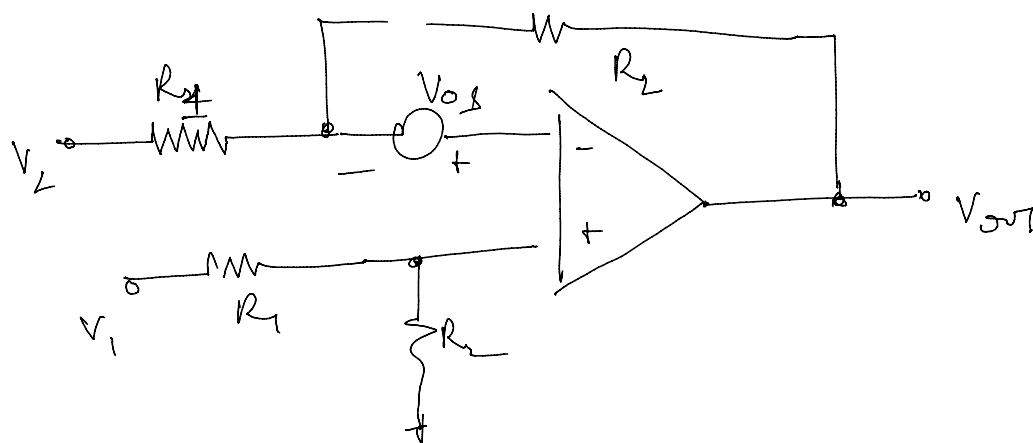


# EFFECT OF OFFSET ON DIFFERENTIAL AMPLIFIER



$$\frac{V_1 R_2}{R_1 + R_2} = \frac{V_{out1} R_1}{R_1 + R_2} + V_{os}$$

$$\text{or } V_{out1} = \frac{V_1 R_2}{R_1} - V_{os} \frac{(R_1 + R_2)}{R_1}$$

$$\frac{V_{out2} - V_2}{R_1 + R_2} \cdot R_1 + V_2 + V_{os} = 0$$

$$V_{out2} = -\frac{V_2 R_2}{R_1} - V_{os} \frac{(R_1 + R_2)}{R_1}$$

$$V_{out} = V_{out1} + V_{out2}$$


$$\Rightarrow V_{out} = (V_1 - V_2) \frac{R_2}{R_1} - \frac{(R_1 + R_2)}{R_1} V_{os}$$

$$\text{or } V_{out} = \left( V_1 - V_2 - V_{os} \frac{(R_1 + R_2)}{R_2} \right) \frac{R_2}{R_1}$$

$$\therefore \text{OFFSEET} = V_{os} \frac{R_1 + R_2}{R_2}$$

# DIFFERENTIAL AMPLIFIER CLOSED LOOP

POLE :

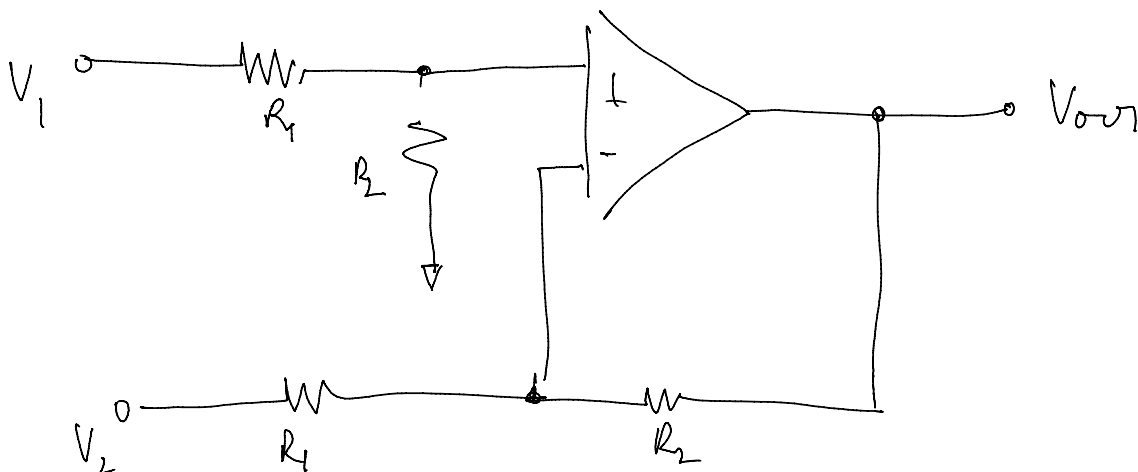

For  $V_2 = 0$

$$V_{out} = \left( V_1 \frac{R_2}{R_1 + R_2} - V_{out} \frac{R_1}{R_1 + R_2} \right) A$$

$$\text{or } V_{out} = \frac{V_1 \frac{R_2}{R_1 + R_2} A}{1 + A \frac{R_1}{R_1 + R_2}}$$

if  $A = \frac{K}{s + p}$  (Dominant pole system)  
(Effectively 1 pole system)

$$V_{out} = \frac{V_1 \frac{R_2 K}{R_1 + R_2}}{s + p + \frac{KR_1}{R_1 + R_2}}$$